

# Sistemas Digitais I

## LESI - 2º ano


### Unit 1 - Introduction

**João Miguel Fernandes**  
www.di.uminho.pt/~jmf
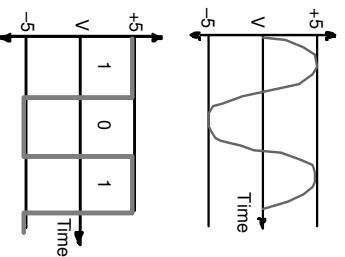
## 1. Introduction

- *Digital vs. Analog Systems (1)* -

- A system is a set of related parts that actuate as a whole to achieve a given goal.
- A system has inputs and outputs and exhibits behaviour characterised by functions that translate inputs into outputs.
- Analog systems process time-varying signals that can take on any value across a continuous range of voltage, current, or ...
- The same applies to digital systems: the difference is that we pretend that they don't.



## 1. Introduction

- *Digital vs. Analog Systems (2)* -

- The critical advantage of digital systems is their ability to deal with electrical signals that have been degraded.
- Due to the discrete nature of the outputs, a slight variation in an input is still interpreted correctly.
- In analog circuits, a slight error at the input generates an error at the output.
- The simplest form of digital system is binary.
- A binary signal is modelled as taking on only two discrete values (0 or 1, LOW or HIGH, False or True).

## 1. Introduction


- *Summary* -

- Digital vs. Analog Systems
- Digital Abstraction
- Synchronous vs. Asynchronous Systems
- Gates
- Flip-flops
- Software tools
- Integrated Circuits
- PLDs
- Digital Design Levels
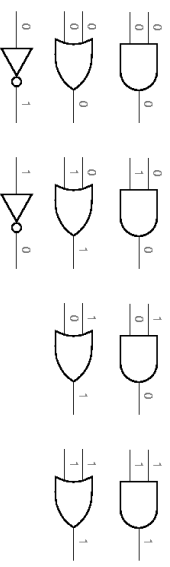
## 1. Introduction

- *Gates* -


- Gates are the most basic digital devices.
- A gate has one or more inputs and produces an output that is a function of the current input values.
- A gate is a combinational circuit because its output depends only on the current input combination.


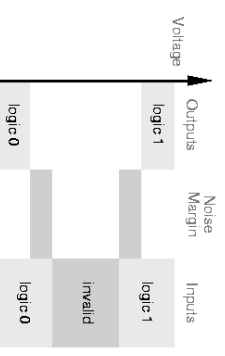
## 1. Introduction

- *Digital Abstraction* -

- Digital circuits deal with analog voltages and currents.
- The digital abstraction allows analog behaviour to be ignored in most cases, so circuits can be modelled as if they really process 0s and 1s.
- Association of a range of analog values with each logic value (0 and 1).
- The difference between the range boundaries is called noise margin.



# 1. Introduction

- *Synchronous vs. Asynchronous Systems* -

- A synchronous system is one whose elements change their values at certain specified times.
- An asynchronous system has outputs that can change at any time.
- As an example, consider a digital alarm clock, which has the alarm set for 13:59.
- In a synchronous system, the outputs all change at the same time: (12:59 → 13:00 → 13:01 → ...).
- In an asynchronous system, outputs are not constrained to change simultaneously: (12:59 → 13:59 → 13:00 → ...).

# 1. Introduction

- *Flip-flops* -

- A flip-flop is a device that store either a 0 or a 1.
- The state of a flip-flop is the value currently stored.
- The stored value can only be changed at certain times, regulated by a "clock" input.
- A digital circuit that contains flip-flops is called a sequential circuit.
- The output of a sequential circuit depend, at any time, not only in its current input but also on the past sequence of inputs that have been applied to it.
- A sequential circuit has memory of past events.

# 1. Introduction

- *Software Tools* -

- Digital design need not involve any software tools.
- Software tools are nowadays an essential part of digital design.
- HDLs (Hardware Description Languages) and the corresponding simulation and synthesis tools are widely used.
- In a CAD (Computer-Aided Design) environment, the tools improve the productivity and help to correct errors and to predict behaviour.
  - Schematic entry;
  - HDLs compilers, simulators and synthesis tools;
  - Timing analysers;
  - Simulators
  - Test benches.

# 1. Introduction


- *Integrated Circuits (ICs)* -

- An IC is a collection of gates fabricated on a single silicon chip.
- ICs are classified by their size:
  - SSI (small scale integration): 1 to 20 gates
  - ANDs, ORs, NOTs.
  - MSI (medium scale integration): 20 to 200 gates
  - decoder, register, counter.
  - LSI (large scale integration): 200 to 200,000 gates
  - small memories, PLDs.
  - VLSI (very large scale integration): > 1.000.000 transistors
  - microprocessors, memories.
- The Pentium 4 has 42.000.000 transistors!!!
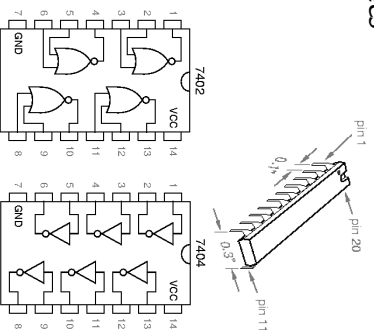
# 1. Introduction

- *SSI ICs* -

- Dual in-line pin (DIP) packages.
- A pin diagram shows the assignment of device signals to package pins.
- Nowadays, SSI ICs are used as "glue" to tie together larger components in complex systems.
- SSI ICs have been largely supplanted by PLDs (Programmable Logic Devices).



# 1. Introduction


- *Programmable Logic Devices (PLDs)* -

- Some ICs can have their logic function "programmed" into them after they are manufactured.
- Most of them can even be reprogrammed, which allows bugs to be corrected without replacing or rewiring the device.
- PLD (PLA or PAL): two-level structure of AND and OR gates with user-programmable connections.
- CPLDs (Complex PLDs) and FPGAs (Field Programmable Gate Arrays) were devised to accommodate larger systems.
- HDLs and the respective tools allow a design to be compiled, synthesised, and downloaded into a device in a short time.
- This permits rapid prototyping to be a reality.
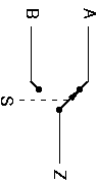
# 1. Introduction

- *Digital Design Levels (1)* -


- Digital design can be carried out at several different levels of representation and abstraction.
- Although one may practice design at a particular level, sometimes he needs to go up and down to understand what is going on.
- The lowest level is device physics and IC manufacturing processes. (not covered by this course)
- The transistor level is the next one. (not covered by this course)
- To explain this and the next levels, consider a multiplexer, with 2 input bits (A, B), 1 control bit (S), and 1 output bit (Z).


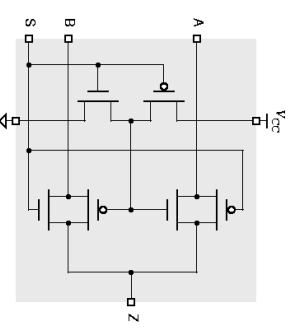
# 1. Introduction

- *Digital Design Levels (2)* -

- For some functions it is advantageous to optimise them by designing at the transistor level.
- The multiplexer can be designed in CMOS technology using transistor circuit structures.
- Using this approach, the multiplexer can be built with just 6 transistors.




# 1. Introduction

- *Digital Design Levels (3)* -

- In traditional logic design, a truth table is used to describe the multiplexer's logic function.
- A truth table lists all possible combinations of input values and the corresponding output values.
- Once a truth table exists, Boolean algebra and minimization algorithms are used to derive an "optimal" 2-level AND-OR equation.
- For the multiplexer:  $Z = S'A + SB$
- This equation can be converted into a gate level logic diagram.


S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

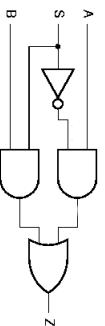
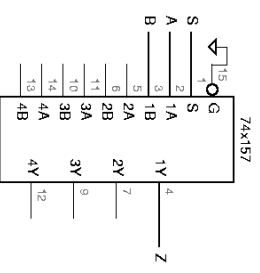
# 1. Introduction

- *Digital Design Levels (4)* -

- For commonly used functions, most digital technologies provide predefined building blocks.
- The 74x157 is an MSI chip that performs multiplexing on 2 4-bit inputs.
- The figure shows the block level diagram for the 74x157 chip.
- The numbers in colour are pin numbers of a 16-pin DIP package containing the device.



# 1. Introduction

- *Digital Design Levels (5)* -

- HDLs, like VHDL, can be used to specify the multiplexer's function at the algorithmic level.
- The entity specifies the inputs and outputs of the circuit.
- The architecture defines the multiplexer behaviour.
- A synthesis tool can process this behavioural description and produce a circuit in a given target technology.

```

Library IEEE;
use IEEE.std_logic_1164.all;

entity Vchaplmux is
    port ( A, B, S: in  STD_LOGIC;
          Z:          out STD_LOGIC );
end Vchaplmux;

architecture Vchaplmux_arch of Vchaplmux is
begin
    Z <= A when S = '0' else B;
end Vchaplmux_arch;

```

- For commonly used functions, most digital technologies provide predefined building blocks.
- The 74x157 is an MSI chip that performs multiplexing on 2 4-bit inputs.
- The figure shows the block level diagram for the 74x157 chip.
- The numbers in colour are pin numbers of a 16-pin DIP package containing the device.

