

Sistemas Digitais I

LESI - 2^o ano

Unit 3 - Boolean Algebra

João Miguel Fernandes

`www.di.uminho.pt/~jmf`



DEP. DE INFORMÁTICA
ESCOLA DE ENGENHARIA
UNIVERSIDADE DO MINHO

3. Boolean Algebra

- Summary -

- Binary Signals
- Combinational vs. Sequential Systems
- Gates
- Switching Algebra
- Axioms
- Theorems
- Duality
- Standard Representation
- Examples

3. Boolean Algebra

- Introduction -

- The success of computer technology is primarily based on simplicity of designing digital circuits and ease of their manufacture.
- Digital circuits are composed of basic processing elements, called gates, and basic memory elements, called flip-flops.
- The simplicity in digital circuit design is due to the fact that input and output signals of each gate or flip-flop can assume only two values, 0 and 1.
- The changes in signal values are governed by laws of Boolean algebra.
- The fact that Boolean algebra is finite and richer in properties than ordinary algebra leads to simple optimisation techniques for functions.
- In order to learn techniques for design of digital circuits, we must understand the properties of Boolean algebra.

3. Boolean Algebra

- *Binary Signals (1)* -

- Digital logic hides the analog world by mapping the infinite set of real values into 2 subsets (0 and 1).
- A logic value, 0 or 1, is often called a binary digit (bit).
- With n bits, 2^n different entities are represented.
- When using electronic circuits, digital designers often use the words “LOW” and “HIGH”, in place of “0” and “1”.
- The assignment of 0 to LOW and 1 to HIGH is called positive logic. The opposite assignment is called negative logic.
- Other technologies can be used to represent bits with physical states.

3. Boolean Algebra

- Binary Signals (2) -

<i>Technology</i>	<i>State Representing Bit</i>	
	<i>0</i>	<i>1</i>
Pneumatic logic	Fluid at low pressure	Fluid at high pressure
Relay logic	Circuit open	Circuit closed
Complementary metal-oxide semiconductor (CMOS) logic	0–1.5 V	3.5–5.0 V
Transistor-transistor logic (TTL)	0–0.8 V	2.0–5.0 V
Fiber optics	Light off	Light on
Dynamic memory	Capacitor discharged	Capacitor charged
Nonvolatile, erasable memory	Electrons trapped	Electrons released
Bipolar read-only memory	Fuse blown	Fuse intact
Bubble memory	No magnetic bubble	Bubble present
Magnetic tape or disk	Flux direction "north"	Flux direction "south"
Polymer memory	Molecule in state A	Molecule in state B
Read-only compact disc	No pit	Pit
Rewritable compact disc	Dye in crystalline state	Dye in noncrystalline state

3. Boolean Algebra


- *Combinational vs. Sequential Systems* -

- A combinational logic system is one whose outputs depend only on its current inputs.
- A combinational system can be described by a truth table.
- The outputs of a sequential logic circuit depend not only on the current inputs but also on the past sequence of inputs \Rightarrow memory.
- A sequential system can be described by a state table.
- A combinational system may contain any number of logic gates but no feedback loops.
- A feedback loop is a signal path of a circuit that allows the output of a gate to propagate back to the input of that same gate.
- Feedback loops generally create sequential circuit behaviour.

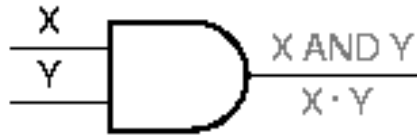3. Boolean Algebra

- Gates (1) -


- Three basic gates (AND, OR, NOT) are sufficient to build any combinational digital logic system. They form a complete set.



X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1



X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

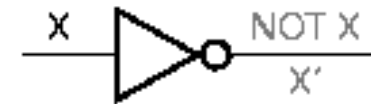


X	NOT X
0	1
1	0

- The symbols and truth tables for AND and OR may be extended to gates with any number of inputs.
- The bubble on the inverter output denotes “inverting” behaviour.

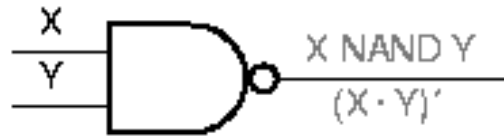
3. Boolean Algebra

- Gates (2) -

- Two more logic functions are obtained by combining NOT with an AND or OR function in a single gate.



X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

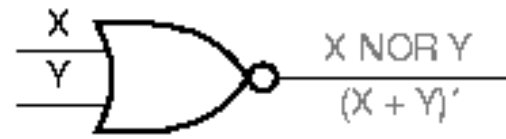


X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

- The symbols and truth tables for NAND and NOR may also be extended to gates with any number of inputs.

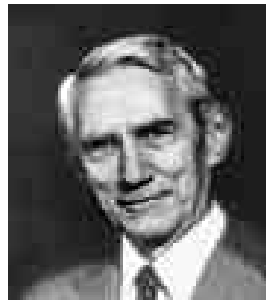3. Boolean Algebra

- *Switching Algebra* -


- In 1854, G. Boole (1815-1865) introduced the formalism that we use for the systematic treatment of logic which is now called Boolean Algebra.
- In 1938, C. Shannon (1916-2001) applied this algebra to prove that the properties of electrical switching circuits can be represented by a 2-valued Boolean Algebra, which is called Switching Algebra.
- Using this algebra, one can formulate propositions that are true or false, combine them to make new propositions and determine if the new propositions are true or false.
- We use a symbolic variable (ex. X) to represent the condition of a logic signal, which is in one of two possible values ("0" or "1").



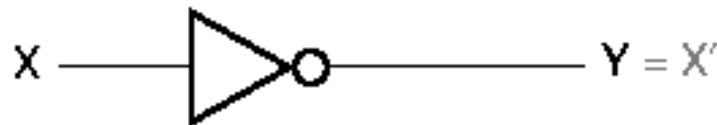3. Boolean Algebra

- Axioms (1) -

- The axioms (or postulates) of a mathematical system are a minimal set of basic definitions that we assume to be true.
- The first axioms embody the digital abstraction:
(A1) $X=0$ if $X \neq 1$ (A1') $X=1$ if $X \neq 0$
- We stated these axioms as a pair, the only difference being the interchange of the symbols 0 and 1.
- This applies to all the axioms and is the basis of duality.
- The next axioms embody the complement notation:
(A2) If $X=0$, then $X'=1$ (A2') If $X=1$, then $X'=0$



- We use a prime (') to denote an inverter's function.

3. Boolean Algebra

- Axioms (2) -

- The last three pairs of axioms state the formal definitions of the AND (logical multiplication) and OR (logical addition) operations:

$$(A3) \quad 0 \cdot 0 = 0$$


$$(A3') \quad 1 + 1 = 1$$

$$(A4) \quad 1 \cdot 1 = 1$$

$$(A4') \quad 0 + 0 = 0$$

$$(A5) \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$(A5') \quad 1 + 0 = 0 + 1 = 1$$

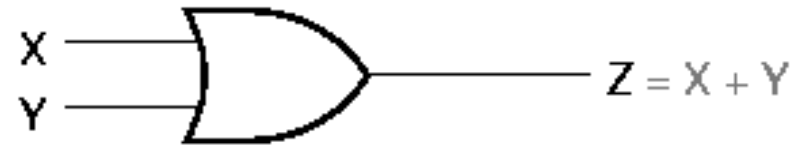

- By convention, in a logic expression involving both multiplication and addition, multiplication has precedence.
- The expression $X \cdot Y + Y \cdot Z'$ is equivalent to $(X \cdot Y) + (Y \cdot Z')$.
- The axioms (A1-A5, A1'-A5') completely define Boolean algebra.

3. Boolean Algebra

- Theorems (1) -

- Theorems are statements, known to be true, that allow us to manipulate algebraic expressions to have simpler analysis or more efficient synthesis of the corresponding circuits.

- Theorems involving a single variable:

(T1) $X+0 = X$	(T1') $X \cdot 1 = X$	(Identities)
(T2) $X+1 = 1$	(T2') $X \cdot 0 = 0$	(Null elements)
(T3) $X+X = X$	(T3') $X \cdot X = X$	(Idempotency)
(T4) $(X')' = X$		(Involution)
(T5) $X+X' = 1$	(T5') $X \cdot X' = 0$	(Complements)

- These theorems can be proved to be true. Let us prove T1:

[X=0] $0+0=0$ (true, according to A4')

[X=1] $1+0=1$ (true, according to A5')

3. Boolean Algebra

- Theorems (2) -

- Theorems involving two or three variables:

$$(T6) \quad X+Y = Y+X \qquad (T6') \quad X \cdot Y = Y \cdot X \qquad \text{(Commutativity)}$$

$$(T7) \quad (X+Y)+Z = X+(Y+Z) \quad (T7') \quad (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) \qquad \text{(Associativity)}$$

$$(T8) \quad X \cdot Y + X \cdot Z = X \cdot (Y+Z) \quad (T8') \quad (X+Y) \cdot (X+Z) = X+Y \cdot Z \qquad \text{(Distributivity)}$$

$$(T9) \quad X+X \cdot Y = X \qquad (T9') \quad X \cdot (X+Y) = X \qquad \text{(Covering)}$$

$$(T10) \quad X \cdot Y + X \cdot Y' = X \qquad (T10') \quad (X+Y) \cdot (X+Y') = X \qquad \text{(Combining)}$$

$$(T11) \quad X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z \qquad \text{(Consensus)}$$

$$(T11') \quad (X+Y) \cdot (X'+Z) \cdot (Y+Z) = (X+Y) \cdot (X'+Z)$$

- Attention to theorem T8' which is not true for integers and reals.
- T9 and T10 are used in the minimisation of logic functions.

3. Boolean Algebra

- Theorems (3) -

- Several important theorems are true for an arbitrary number of variables.

- Theorems involving n variables:

$$(T12) X+X+ \dots +X = X$$

Generalised Idempotency

$$(T12') X \cdot X \cdot \dots \cdot X = X$$

$$(T13) (X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$$

DeMorgan's theorems

$$(T13') (X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$$

$$(T14) [F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$$

Generalised DeMorgan's th.

$$(T15) F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$$

Shannon's

$$(T15') F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$$

expansion

theorems

3. Boolean Algebra

- Theorems (4) -

- DeMorgan's theorem (T13 and T13') for n=2:
 $(X \cdot Y)' = X' + Y'$
 $(X + Y)' = X' \cdot Y'$
- DeMorgan's theorem gives a procedure for complementing a logic function.
- DeMorgan's theorem can be used to convert AND/OR expressions to OR/AND expressions.

- Example:

$$Z = A' B' C + A' B C + A B' C + A B C'$$

$$Z' = (A + B + C') \cdot (A + B' + C') \cdot (A' + B + C') \cdot (A' + B' + C)$$











Augustus De Morgan
(1806-1871)

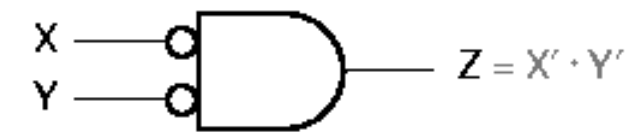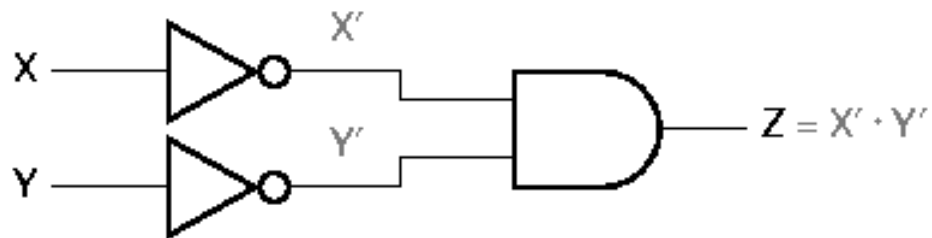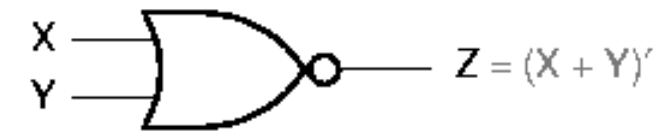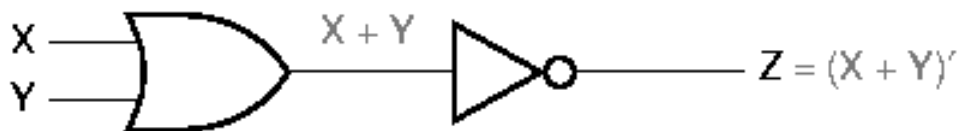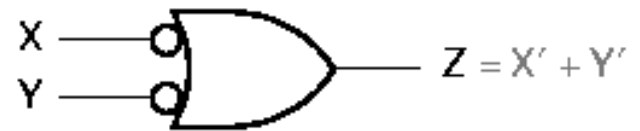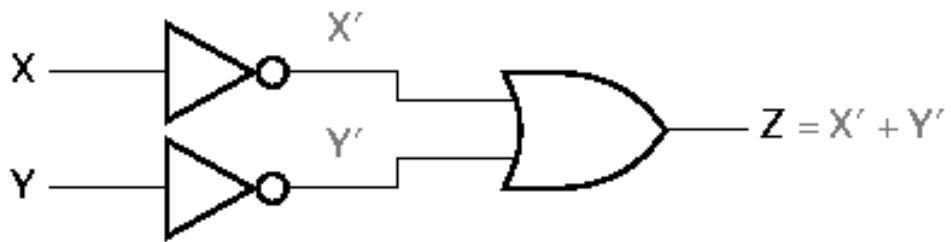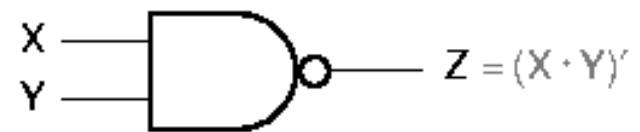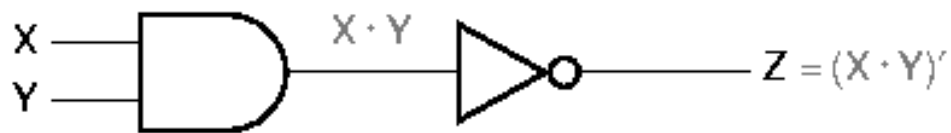3. Boolean Algebra

- Theorems (5) -

Equivalent gates according to DeMorgan's theorem



3. Boolean Algebra

- Theorems (6) -

- Since Boolean algebra has only two elements, we can also show the validity of these theorems by using truth tables.
- To do this, a truth table is built for each side of the equation that appears in the theorem.
- Then both sides of the equation are checked to see if they yield identical results for all the combinations of variable values.
- Let us prove DeMorgan's theorem (T13 and T13') for n=2:

$$(X+Y)' = X' \cdot Y'$$

$$(X \cdot Y)' = X' + Y'$$

X	Y	\bar{X}	\bar{Y}	$\overline{X+Y}$	$\bar{X} \cdot \bar{Y}$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

X	Y	\bar{X}	\bar{Y}	$\overline{X \cdot Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

3. Boolean Algebra

- Duality (1) -

- Theorems were presented in pairs.
- The prime version of a theorem is obtained from the unprimed version by swapping “0” and “1”, and “·” and “+”.
- Principle of Duality: Any theorem or identity in Boolean algebra remains true if 0 and 1 are swapped and · and + are swapped throughout.
- Duality is important because it doubles the usefulness of everything about Boolean algebra and manipulation of logic functions.
- The dual of a logic expression is the same expression with + and · swapped:
$$F^D(X_1, X_2, \dots, X_n, +, \cdot, ') = F(X_1, X_2, \dots, X_n, \cdot, +, ')$$
- Do not confuse duality with DeMorgan's theorems!
$$[F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$$
$$[F(X_1, X_2, \dots, X_n)]' = F^D(X_1', X_2', \dots, X_n')$$

3. Boolean Algebra

- Duality (2) -




X	Y	Z
LOW	LOW	LOW
LOW	HIGH	LOW
HIGH	LOW	LOW
HIGH	HIGH	HIGH

Electric function




X	Y	Z
LOW	LOW	LOW
LOW	HIGH	HIGH
HIGH	LOW	HIGH
HIGH	HIGH	HIGH

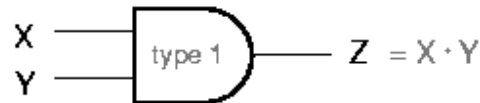

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Positive-logic

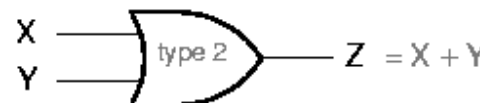


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1



X	Y	Z
1	1	1
1	0	1
0	1	1
0	0	0

Negative-logic

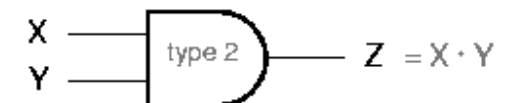


X	Y	Z
1	1	1
1	0	0
0	1	0
0	0	0


3. Boolean Algebra

- Duality (3) -

- Positive-logic

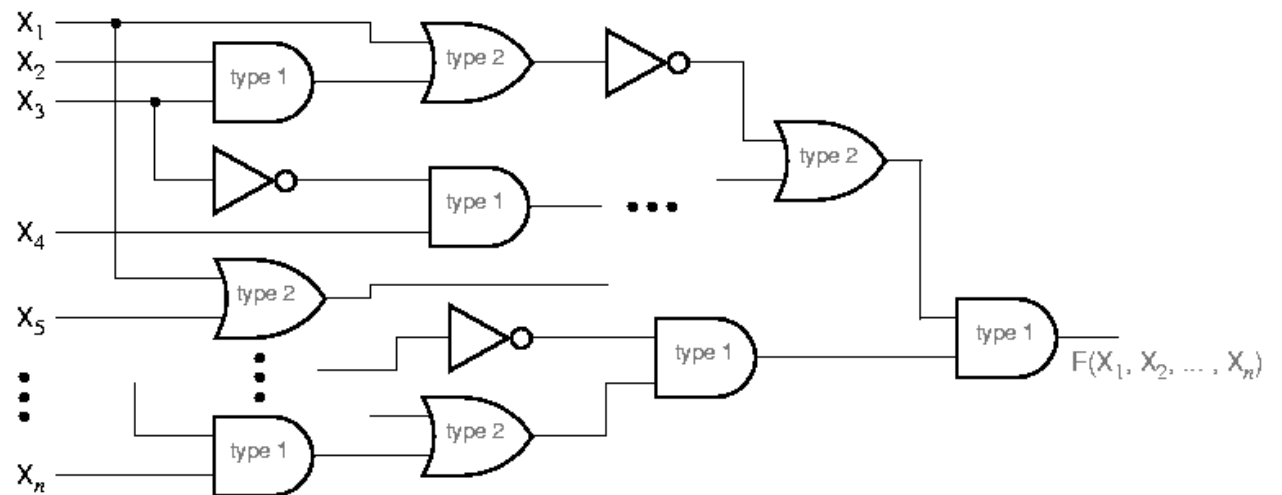

- Negative-logic

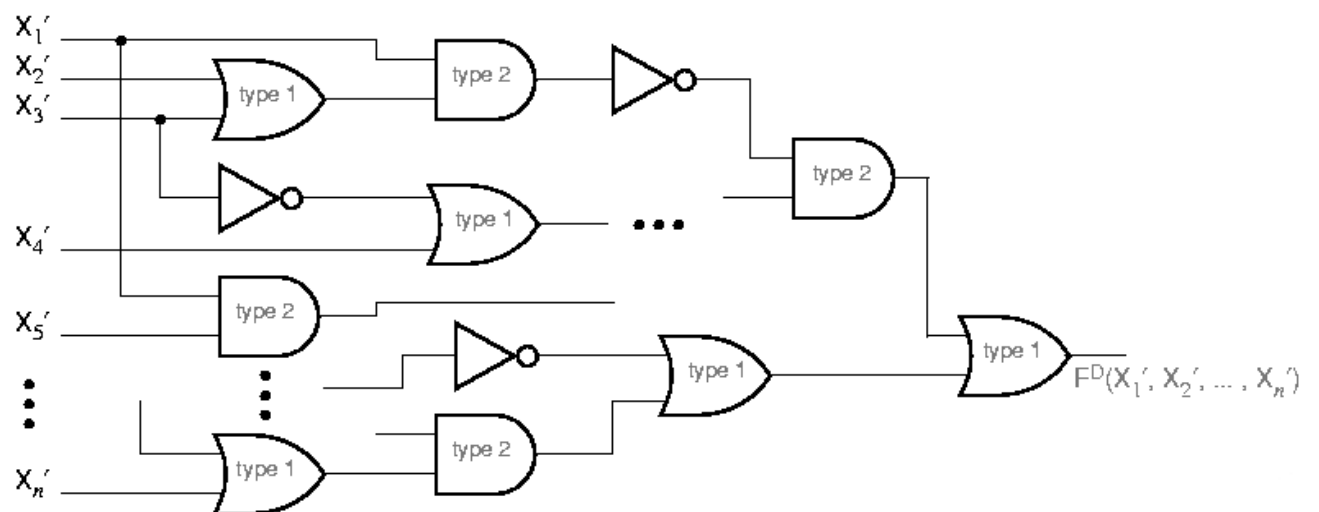

3. Boolean Algebra

- Standard Representation (1) -

- The most basic representation of a logic function is a truth table.
- A truth table lists the output of the circuit for every possible input combination.
- There are 2^n rows in a truth table for an n-variable function.

<i>Row</i>	X	Y	Z	F
0	0	0	0	F(0,0,0)
1	0	0	1	F(0,0,1)
2	0	1	0	F(0,1,0)
3	0	1	1	F(0,1,1)
4	1	0	0	F(1,0,0)
5	1	0	1	F(1,0,1)
6	1	1	0	F(1,1,0)
7	1	1	1	F(1,1,1)

<i>Row</i>	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

- There are 2^8 ($8=2^3$) different logic functions for 3 variables.

3. Boolean Algebra

- *Standard Representation (2)* -

- Truth tables can be converted to algebraic expressions.
- A literal is a variable or the complement of a variable. Ex: X , Y , X' .
- A product term is a single literal or a logical product of two or more literals. Ex: Z' , $W \cdot X \cdot Y$, $W \cdot X' \cdot Y'$.
- A sum-of-products (SOP) is a logical sum of product terms.
Ex: $Z' + W \cdot X \cdot Y$.
- A sum term is a single literal or a logical sum of two or more literals. Ex: Z' , $W + X + Y$, $W + X' + Y'$.
- A product-of-sums (POS) is a logical product of sum terms.
Ex: $Z' \cdot (W + X + Y)$.

3. Boolean Algebra

- *Standard Representation (3)* -

- A normal term is a product or sum term in which no variable appears more than once.
Examples (**non**-normal terms): $W \cdot X \cdot X' \cdot Z'$, $W' + Y' + Z + W'$.
- A n-variable minterm is a normal product term with n literals. Examples (with 4 variables): $W \cdot X \cdot Y \cdot Z'$, $W' \cdot X' \cdot Y \cdot Z$.
- A n-variable maxterm is a normal sum term with n literals. Examples (with 4 variables): $W + X + Y + Z'$, $W' + X' + Y + Z$.
- There is a correspondence between the truth table and minterms and maxterms.
- A minterm is a product term that is 1 in one row of the truth table.
- A maxterm is a sum term that is 0 in one row of the truth table.

3. Boolean Algebra

- *Standard Representation (4)* -

Minterms and maxterms for a 3-variable function $F(X,Y,Z)$

Row	X	Y	Z	F	Minterm	Maxterm
0	0	0	0	$F(0,0,0)$	$X' \cdot Y' \cdot Z'$	$X + Y + Z$
1	0	0	1	$F(0,0,1)$	$X' \cdot Y' \cdot Z$	$X + Y + Z'$
2	0	1	0	$F(0,1,0)$	$X' \cdot Y \cdot Z'$	$X + Y' + Z$
3	0	1	1	$F(0,1,1)$	$X' \cdot Y \cdot Z$	$X + Y' + Z'$
4	1	0	0	$F(1,0,0)$	$X \cdot Y' \cdot Z'$	$X' + Y + Z$
5	1	0	1	$F(1,0,1)$	$X \cdot Y' \cdot Z$	$X' + Y + Z'$
6	1	1	0	$F(1,1,0)$	$X \cdot Y \cdot Z'$	$X' + Y' + Z$
7	1	1	1	$F(1,1,1)$	$X \cdot Y \cdot Z$	$X' + Y' + Z'$

3. Boolean Algebra

- *Standard Representation (5)* -

- An n-variable minterm can be represented by an n-bit integer (the minterm number).
- In minterm i , a variable appears complemented if the respective bit in the binary representation of i is 0; otherwise it is uncomplemented.
- For example, row 5 (101) is related to minterm $X \cdot Y' \cdot Z$.
- In maxterm i , a variable appears complemented if the corresponding bit in the binary representation of i is 1; otherwise it is unprimed.
- For example, row 5 (101) is related to maxterm $X' + Y + Z'$.
- To specify the minterms and maxterms, it is mandatory to know the number of variables in the function and their order.

3. Boolean Algebra

- Standard Representation (6) -

- Based on the correspondence between the truth table and the minterms, an algebraic representation of a logic function can be created.
- The canonical sum of a logic function is a sum of the minterms corresponding to truth table rows for which the function is 1.

Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

- From the table:

$$F = \sum_{X,Y,Z} (0,3,4,6,7) = X' \cdot Y' \cdot Z' + X' \cdot Y \cdot Z + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z' + X \cdot Y \cdot Z$$

- The notation $\sum_{X,Y,Z} (0,3,4,6,7)$ is a minterm list and means the sum of minterms 0,3,4,6, and 7, with variables X, Y, and Z.
- The minterm list is also known as the on-set for the logic function.

3. Boolean Algebra

- Standard Representation (7) -

- Based on the correspondence between the truth table and the maxterms, an algebraic representation of a logic function can be created.
- The canonical product of a function is a product of the maxterms corresponding to input combinations for which the function is 0.
- From the table:
$$F = \prod_{X,Y,Z} (1,2,5) = (X+Y+Z') \cdot (X+Y'+Z) \cdot (X'+Y+Z')$$
- The notation $\prod_{X,Y,Z} (1,2,5)$ is a maxterm list and means the product of maxterms 1,2, and 5, with variables X, Y, and Z.
- The maxterm list is also known as the off-set for the logic function.

Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

3. Boolean Algebra

- *Standard Representation (8)* -

- It is easy to convert between a minterm list and a maxterm list.
- For a function of n variables, the minterms and maxterms are in the set $\{0, 1, \dots, 2^n-1\}$.
- A minterm or maxterm list contains a subset of these numbers.
- To switch between the lists, one takes the set complement.
- Examples:

$$\sum_{A,B,C} (0,1,2,3) = \prod_{A,B,C} (4,5,6,7)$$

$$\sum_{X,Y} (1) = \prod_{X,Y} (0,2,3)$$

$$\sum_{W,X,Y,Z} (1,2,3,5,8,12,13) = \prod_{W,X,Y,Z} (0,4,6,7,9,10,11,14,15)$$

3. Boolean Algebra

- *Standard Representation (9)* -

- We have learned 5 possible representations for a combinational logic function.
 - **A truth table;**
 - **An algebraic sum of minterms (the canonical sum);**
 - **A minterm list, using the Σ notation;**
 - **An algebraic product of maxterms (the canonical product);**
 - **A maxterm list, using the Π notation;**
- Each one of these representations specifies exactly the same information.
- Given any of them, we can derive the other four using a simple mechanical process.

3. Boolean Algebra

- Examples (1) -

- Ex.1: Let $F = X \cdot Y + X \cdot Y' \cdot Z + X' \cdot Y \cdot Z$. Derive the expression for F' in the product of sums form.
- $$\begin{aligned} F' &= (XY + XY'Z + X'YZ)' \\ &= (XY)' \cdot (XY'Z)' \cdot (X'YZ)' \\ &= (X' + Y') (X' + Y + Z') (X + Y' + Z') \end{aligned}$$
- Ex.2: Express the function $G(X,Y,Z) = X + Y \cdot Z$ as a sum of minterms.
- $$\begin{aligned} G &= X + Y \cdot Z \\ &= X \cdot (Y + Y') \cdot (Z + Z') + Y \cdot Z \cdot (X + X') \\ &= XYZ + XYZ' + XY'Z + XY'Z' + XYZ + X'YZ \\ &= X'YZ + XY'Z' + XY'Z + XYZ' + XYZ \\ &= \sum_{X,Y,Z} (3,4,5,6,7) \end{aligned}$$

3. Boolean Algebra

- Examples (2) -

- Ex.3: Derive the product-of-maxterms form for $H = X' \cdot Y' + X \cdot Z$.

- $$\begin{aligned} H &= X' Y' + XZ \\ &= (X' Y' + X) (X' Y' + Z) \\ &= (X' + X) (Y' + X) (X' + Z) (Y' + Z) \\ &= (X + Y') (X' + Z) (Y' + Z) \end{aligned}$$

- Each OR term in the expression is missing one variable:

- $X + Y' = X + Y' + Z Z' = (X + Y' + Z) (X + Y' + Z')$

- $X' + Z = X' + Z + Y Y' = (X' + Y + Z) (X' + Y' + Z)$

- $Y' + Z = Y' + Z + X X' = (X + Y' + Z) (X' + Y' + Z)$

- Finally we combine these terms:

$$H = (X + Y' + Z) (X + Y' + Z') (X' + Y + Z) (X' + Y' + Z)$$

$$\prod_{X,Y,Z} (2,3,4,6)$$

3. Boolean Algebra

- Examples (3) -

- Ex.4: Derive the product-of-maxterms form for $H = X' \cdot Y' + X \cdot Z$.

X	Y	Z	H
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- From the table, we obtain:

$$H = \prod_{X,Y,Z} (2,3,4,6)$$

$$H = \sum_{X,Y,Z} (0,1,5,7)$$

- Compare this solution with the solution of ex.3.

- Ex.5: Derive a standard form with a reduced number of operators for $J = XYZ + XYZ' + XY'Z + X'YZ$.

$$\begin{aligned} J &= XYZ + XYZ' + XY'Z + X'YZ \\ &= XY(Z+Z') + X(Y+Y')Z + (X+X')YZ \\ &= XY+XZ+YZ \end{aligned}$$