

Sistemas Digitais I

LESI - 2º ano


Unit 6 - Combinational Design Practices

João Miguel Fernandes
www.di.uminho.pt/~jmf

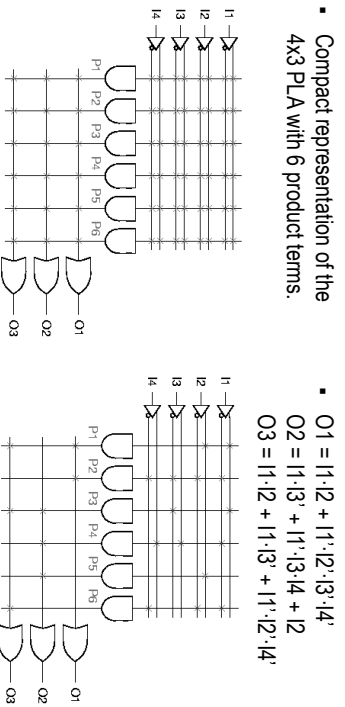6. Combinational Practices

- PLDs (1) -

- The first PLDs were Programmable Logic Arrays (PLAs).
- A PLA is a combinational, 2-level AND-OR device that can be programmed to realise any sum-of-products logic expression.
- A PLA is limited by:
 - the number of inputs (n)
 - the number of outputs (m)
 - the number of product terms (p)
- We refer to an "n x m PLA with p product terms". Usually, $p \ll 2^n$.
- An n x m PLA with p product terms contains p 2n-input AND gates and m p-input OR gates.



6. Combinational Practices


- Summary -

- PLDs
- Decoders
- 7-Segment Decoders
- Encoders
- Multiplexers
- XOR and Parity Circuits
- Comparators
- Adders, Subtractors and ALUs
- Multipliers

 6. Combinational Practices

- PLDs (2) -


- Each input is connected to a buffer that produces a true and a complemented version of the signal.
- Potential connections are indicated by Xs.
- The device is programmed by establishing the needed connections.
- The connections are made by fuses.



 6. Combinational Practices

- PLDs (4) -


- Another PLD is PAL (Programmable Array Logic).
- A PAL device has a fixed OR array.
- In a PAL, product terms are not shared by the outputs.
- Each output has a fixed and unique set of product terms that it can use.
- A PAL is usually faster than a similar PLA.



 6. Combinational Practices

- PLDs (5) -


- Part of the logic diagram of the PAL 16L8.



 6. Combinational Practices

- Decoders (2) -

- A 74x139 IC has two independent 2-to-4 decoders.




Inputs				Outputs			
G _L	B	A	V ₀ L	V ₂ L	V ₁ L	V ₀ L	V ₀ L
0	x	x	1	1	1	1	1
0	0	0	1	1	0	1	0
0	0	1	1	0	1	1	1
0	1	0	1	0	0	1	1
0	1	1	0	1	1	1	1

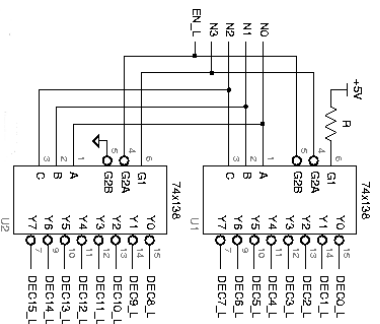6. Combinational Practices

- Decoders (4) -

- Multiple decoders can be used to decode larger code words.
- The top decoder (U1) is enabled when N3 is 0, and the bottom decoder (U2) is enabled when N3 is 1.
- To handle larger code words, decoders can be cascaded hierarchically.





6. Combinational Practices

- Decoders (1) -

- A decoder is a circuit that converts coded inputs into coded outputs.
- Usually, the input code has fewer bits than the output code.
- The most common decoder is an n-to-2ⁿ or binary decoder.
- A binary decoder is used when one of 2ⁿ outputs needs to be activated based on an n-bit input value.


Inputs				Outputs			
EN	I1	I0	V ₃	V ₂	V ₁	V ₀	V ₀
0	x	x	0	0	0	0	0
1	0	0	0	0	1	0	0
1	0	1	0	1	0	0	0
1	1	0	1	0	0	0	0
1	1	1	1	0	0	0	0

  

6. Combinational Practices

- Decoders (3) -

- A 74x138 IC has one 3-to-8 decoder.

 


Inputs							Outputs							
G1	G2A_L	G2B_L	C	B	A	V ₇ L	V ₆ L	V ₅ L	V ₄ L	V ₃ L	V ₂ L	V ₁ L	V ₀ L	
0	x	x	x	x	x	1	1	1	1	1	1	1	1	
0	1	x	x	x	x	1	1	1	1	1	1	1	1	
x	0	0	0	0	0	1	1	1	1	1	1	1	1	
x	0	0	0	1	0	1	1	1	1	1	1	1	1	
x	0	0	1	0	1	1	1	1	1	1	1	1	1	
x	0	1	0	0	0	1	1	1	1	1	1	1	1	
x	0	1	0	1	0	1	1	1	1	1	1	1	1	
x	1	0	0	0	0	1	1	1	1	1	1	1	1	
x	1	0	0	1	0	1	1	1	1	1	1	1	1	
x	1	0	1	0	0	1	1	1	1	1	1	1	1	
x	1	0	1	1	0	1	1	1	1	1	1	1	1	
x	1	1	0	0	0	1	1	1	1	1	1	1	1	
x	1	1	0	1	0	1	1	1	1	1	1	1	1	
x	1	1	1	0	0	1	1	1	1	1	1	1	1	
x	1	1	1	1	0	1	1	1	1	1	1	1	1	

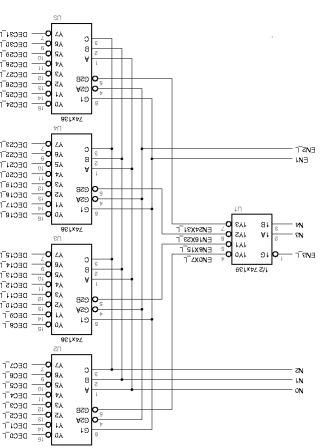6. Combinational Practices

- Decoders (5) -

- To handle larger code words, decoders can be cascaded hierarchically.
- A 5-to-32 decoder can be built with one 2-to-4 and four 3-to-8 decoders.
- The 2-to-4 decoder treats the high order bits.
- The 3-to-8 decoders treat the low-order bits.



6. Combinational Practices

- Decoders (6) -

- There are several ways to write decoders in VHDL.
- The most primitive would be to write a structural description equivalent to the logic circuit on slide 7.

```
library IEEE;
use IEEE.std_logic_1164.all;

entity decoder_7 is
    port (
        A: in STD_LOGIC;
        Y0, Y1, Y2, Y3: out STD_LOGIC );
end decoder_7;

architecture VHDLdec_7 of VHDLdec_7 is
    component sev_seg_7
        port (
            A: in STD_LOGIC;
            component and7: port (
                I0, I1, I2: in STD_LOGIC;
                O: out STD_LOGIC );
            end component;
        end component;
    begin
        sev_seg_7: sev_seg_7 (A, and7);
        and7: and7 port map (
            O0(0), O1(1), O2(2), O3(3), O4(4), O5(5), O6(6), O7(7));
    end VHDLdec_7;
```

6. Combinational Practices

- Decoders (8) -

- Another alternative is using the behavioral style.

```
architecture VHDLdec_8 of VHDLdec_8 is
begin
    process (G1, G2, G3, A)
    begin
        Y <= "00000000";
        if (G1 and G2 and G3) = '1' then
            for i in 0 to 7 loop
                Y(i) <= not A;
            end loop;
        end process;
    end VHDLdec_8;
```

Inputs							Outputs						
A	B	C	D	E	F	G	a	b	c	d	e	f	g
0	x	x	x	x	x	x	0	0	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	1	0	1	0	0
1	0	0	1	0	1	1	0	1	1	0	1	0	0
1	0	0	1	0	1	0	1	1	1	0	1	0	1
1	0	1	0	1	1	1	0	1	1	0	1	0	1
1	0	1	0	1	1	0	1	1	0	1	1	0	1
1	0	1	1	0	1	1	0	1	1	1	0	1	1
1	0	1	1	0	1	1	1	0	1	1	1	0	1
1	0	1	1	1	0	1	1	1	1	1	1	1	1
1	0	1	1	1	0	0	0	0	0	0	0	0	0
1	1	0	0	1	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	0	1	1	1	0	1	1	1
1	1	0	1	0	1	1	0	1	1	0	1	1	1
1	1	0	1	0	1	0	1	0	0	1	0	1	1
1	1	0	1	1	0	0	1	0	0	1	0	1	1
1	1	1	0	1	0	0	0	1	1	0	1	1	1
1	1	1	1	0	0	0	1	1	1	1	1	1	1

6. Combinational Practices

- 7-Segment Decoders (2) -

- Exercise 1: Obtain minimised expressions for outputs of the 7-segment decoder.
- Exercise 2: Write a VHDL description of a 7-segment decoder.

6. Combinational Practices

- Decoders (7) -

- The second alternative is using the dataflow style.

```
library IEEE;
use IEEE.std_logic_1164.all;


entity VHDL13_8 is
    port (
        A: in STD_LOGIC;
        B: in STD_LOGIC_VECTOR (2 downto 0);
        Y_L: out STD_LOGIC_VECTOR (6 to 1) );
end VHDL13_8;

architecture VHDL13_8 of VHDL13_8 is
    signal Y_L_1: STD_LOGIC_VECTOR (6 to 1);
begin
    Y_L_1 <= (others => '0');
    Y_L_1(6) <= not A;
    Y_L_1(5) <= not B(2);
    Y_L_1(4) <= not B(1);
    Y_L_1(3) <= not B(0);
    Y_L_1(2) <= not B(2) and not B(1);
    Y_L_1(1) <= not B(2) and not B(0);
end VHDL13_8;
```

 6. Combinational Practices

- 7-Segment Decoders (1) -

- A 7-segment display is used in watches, calculators, and devices to show decimal data.
- A digit is displayed by illuminating a subset of the 7 line segments.




- A 7-segment decoder has a 4-bit BCD as its input and the 7-segment code as its output.

 6. Combinational Practices

- Encoders (1) -


- An encoder is a circuit whose output code has normally fewer bits than its input code.
- The simplest encoder to build is a 2^n -to- n or binary encoder. It has the opposite function as a binary decoder.
- Equations for an 8-to-3 encoder :
 - $Y_0 = I_1 + I_3 + I_5 + I_7$
 - $Y_1 = I_2 + I_3 + I_6 + I_7$
 - $Y_2 = I_4 + I_5 + I_6 + I_7$
- Only 1 input is active at a time. What happens if 2 inputs are asserted (ex: I2 and I4)?



 6. Combinational Practices

- Encoders (2) -


- To implement a request encoder, the binary encoder does not work!
- It assumes that only 1 input is asserted.



- If multiple requests can be made simultaneously, a priority must be assigned to the input lines.
- When multiple requests are made, the device (priority encoder) produces the number of the highest-priority requestor.

6. Combinational Practices


- Encoders (3) -

 

- Input 17 has the highest priority.
- Outputs A2-A0 contain the number of the highest-priority asserted input, if any.
- The IDLE output is asserted if no inputs are asserted.
- Intermediate variable H_i is 1, if i is the highest priority 1-input:
 - $H7 = 17$
 - $H6 = 16 \cdot 17'$
 - $H5 = 15 \cdot 16' \cdot 17'$
 - $H4 = 14 \cdot 15' \cdot 16' \cdot 17'$
 - ... (similar equations for H3-H0)
- $A0 = H1 + H3 + H5 + H7$
 - $A1 = H2 + H3 + H6 + H7$
 - $A2 = H4 + H5 + H6 + H7$
 - $IDLE = 10' \cdot 11' \cdot 12' \cdot 13' \cdot 14' \cdot 15' \cdot 16' \cdot 17'$

6. Combinational Practices


- Multiplexers (1) -

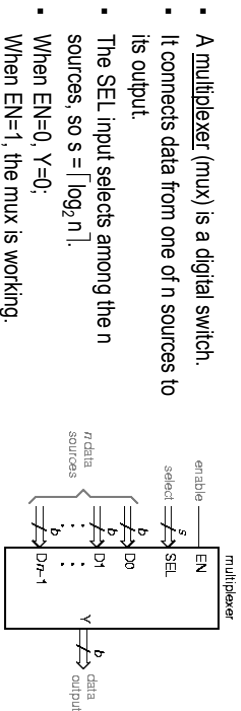

- A multiplexer (mux) is a digital switch.
- It connects data from one of n sources to its output.
- The SEL input selects among the n sources, so $s = \lceil \log_2 n \rceil$.
- When $EN=0$, $Y=0$;
- When $EN=1$, the mux is working.
- Multiplexers are used in computers between the processor's registers and its ALU, to select among a set of registers which one is connected to the ALU.

6. Combinational Practices

- Multiplexers (2) -

 

Inputs				Outputs			
EN	L	C	B	A	Y	Y _L	Y _H
1	X	X	X	X	0	1	
0	0	0	0	0	D0	D0'	
0	0	0	0	1	D1	D1'	
0	0	0	1	0	D2	D2'	
0	0	1	1	0	D3	D3'	
0	1	0	0	0	D4	D4'	
0	1	0	1	0	D5	D5'	
0	1	1	0	0	D6	D6'	
0	1	1	1	1	D7	D7'	

- A 74x151 IC has one 8-bit input, 1-bit multiplexer.
- The select inputs are named A,B,C, where C is the MSB.
- The enable input EN_L is active low.
- Both active-low and high versions of the output are provided

6. Combinational Practices

- Multiplexers (3) -




Inputs				Outputs			
G_L	S	1Y	2Y	3Y	4Y		
1	X	0	0	0	0	0	0
0	0	1A	2A	3A	4A		
0	1	1B	2B	3B	4B		


- A 74x157 IC has one 2-input, 4-bit multiplexer.
- The select input is S.
- The enable input G_L is active low.
- The truth table was extended and inputs appear at the outputs columns.

6. Combinational Practices

- Multiplexers (4) -

 

 - A multiplexer can be used to select one of n sources of data to transmit on a bus.
- At the other end, a demultiplexer can be used to route the bus to one of m destinations.
- The function of a multiplexer is the inverse of a demultiplexer's.
- A 1-bit, n -output demultiplexer has one data input and s inputs to select one of the $n=2^s$ data outputs.



6. Combinational Practices

- Multiplexers (5) -

- It is easy to describe multiplexers in VHDL.
- In the dataflow style, a SELECT statement is required.

```

library IEEE;
use IEEE.std_logic_1164.all;

entity mux16b is
    port (
        S: in std_logic_vector (3 downto 0); -- Select inputs, 0-2 = m, A-D
        A: in std_logic_vector (15 to 0); -- Data A output
        B: in std_logic_vector (15 to 0); -- Data B output
    );
end mux16b;

architecture mux16b of mux16b is
begin
    with S select Y <=
        A when "00",
        B when "01",
        C when "10",
        D when "11",
        (others => '0') when others; -- this creates an 8-bit vector of '0'
end mux16b;
    
```

6. Combinational Practices

- XOR and Parity Circuits (1) -


- An Exclusive-OR (XOR) gate is a 2-input gate whose output is 1, if exactly one of its inputs is 1.

X	Y	$X \oplus Y$ (XOR)	$(X \oplus Y)$ (XNOR)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1
- An XOR gate produces a 1 output if its input are different.
- An Exclusive-NOR (XNOR) is just the opposite: it produces a 1 output if its inputs are the same.
- The XOR operation is denoted by the symbol \oplus .
- $X \oplus Y = X'Y + XY'$

 6. Combinational Practices

- XOR and Parity Circuits (3) -

- n XOR gates may be cascaded to form a circuit with n+1 inputs and a single output. This is a odd-parity circuit, because its output is 1 if an odd number of its inputs are 1.
- If the output of either circuit is inverted, we get an even-parity circuit, whose output is 1 if an even number of its inputs are 1.



6. Combinational Practices

- Multiplexers (6) -

- In a behavioural architecture, a CASE statement is used.

```


architecture mux16b of mux16b is
begin
    process(S, A, B, C, D)
    begin
        case S is
            when "00" => Y <= A;
            when "01" => Y <= B;
            when "10" => Y <= C;
            when "11" => Y <= D;
        when others => Y <= (others => '0'); -- 8-bit vector of '0'
        end process;
    end mux16b;
end mux16b;
    
```

- It is easy to customise the selection criteria in a VHDL multiplexer program.

 6. Combinational Practices

- XOR and Parity Circuits (2) -

- There are 4 symbols for each XOR and XNOR function.



- These alternatives are a consequence of the following rule:
 - Any two signals (inputs or output) of an XOR or XNOR gate may be complemented without changing the resulting logic function.
- In bubble-to-bubble design we choose the symbol that is most expressive of the logic function being performed.

6. Combinational Practices

- XOR and Parity Circuits (4) -

- VHDL provides the primitive operators XOR and XNOR.
- A 3-input XOR device can be specified in VHDL dataflow style program.

```

library IEEE;
use IEEE.std_logic_1164.all;

entity xor3 is
    port (A, B, C: in std_logic;
        Y: out std_logic);
end xor3;

architecture xor3 of xor3 is
begin
    Y <= A xor B xor C;
end xor3;
    
```

6. Combinational Practices

- XOR and Parity Circuits (5) -

- A 9-input parity function can be specified behaviourally.

```

library IEEE;
use IEEE.std_logic_1164.all;

entity parity9 is
    port (i: in std_logic_vector (1 to 9));
         out: out std_logic);
end parity9;

architecture parity9p of parity9 is
begin
    process (i)
        variable p : std_logic;
    begin
        p := i(1);
        for j in 2 to 9 loop
            if i(j) = '1' then p := not p; end if;
        end loop;
        out := p;
    end process;
end parity9p;
    
```

6. Combinational Practices

- Comparators (1) -


- Comparing two binary words is a common operation in computers.
- A circuit that compares 2 binary words and indicates whether they are equal is a comparator.
- Some comparators interpret their input as signed or unsigned numbers and also indicate an arithmetic relationship (greater or less than) between the words.
- These circuits are often called magnitude comparators.
- XOR and XNOR gates can be viewed as 1-bit comparators.
- The DIFF output is asserted if the inputs are different.



 6. Combinational Practices

- Comparators (2) -

- The outputs of 4 XOR gates can be ORed to create a 4-bit comparator.




- The DIFF output is asserted if any of the input-bit pairs are different.
- This circuit can be easily adapted to any number of bits per word.

 6. Combinational Practices

- Comparators (3) -

- An iterative circuit is a combinational circuit with the following structure.





- The circuit contains n identical modules, each of which has both primary inputs and outputs and cascading inputs and outputs.
- The left-most cascading inputs are usually connected to fixed values.

6. Combinational Practices

- Comparators (4) -

- Two n-bit values X and Y can be compared one bit at a time using a single bit EQ_i at each step to keep track of whether all of the bit-pairs have been equal so far:

  
- Set EQ₀ to 1 and set i to 0.
- If EQ_i is 1 and X=Y_i, set EQ_{i+1} to 1. Else set EQ_{i+1} to 0.
- Increment i.
- If i < n, go to step 2.



 6. Combinational Practices

- Comparators (5) -


- Several MSI comparators have been developed commercially.
- The 74x85 is a 4-bit comparator.
- It provides a greater-than output, a less-than output and an equal output.
- The 74x85 also has cascading inputs for combining multiple chips to create comparators for more than 4 bits.
- AGTBOUT = (A>B) + (A=B) · AGTBIN
- AEOBOUT = (A=B) · AEOBIN
- ALTBOUT = (A<B) + (A=B) · ALTBIN



 6. Combinational Practices

- Comparators (6) -

- With three 74x85 circuits, a 12-bit comparator can be built.



6. Combinational Practices

- Comparators (7) -

- VHDL has comparison operators for all of its built-in types.
- Equality ($=$) and inequality (\neq) operators apply to all types.
- For array and record types, the operands must have equal size and structure, and the operands are compared component by component.
- VHDL's other comparison operators ($>$, $<$, $>=$, $<=$) apply only to integers, enumerated types and one-dimensional arrays of enumeration or integer types.

6. Combinational Practices

- Adders, Subtractors and ALUs (1) -

- Addition is the most commonly performed arithmetic operation in digital systems.
- An adder combines two arithmetic operands using the addition rules.
- The same addition rules, and hence the same adders, are used for both unsigned and 2's complement numbers.
- An adder can perform subtraction as the addition of the minuend and the complemented subtrahend.
- A subtractor can also be built to perform subtraction directly.
- An ALU (Arithmetic and Logic Unit) performs addition, subtraction, and other logical operations.

6. Combinational Practices

- Adders, Subtractors and ALUs (2) -

- The simplest adder, called a half adder, adds two 1-bit operands X and Y, producing a 2-bit sum.
- The sum can range from 0 to 2, which requires two bits to express.
- The low-order bit of the sum may be named HS (half sum).
- The high-order bit of the sum may be named CO (carry out).
- The following equations can be written:

$$HS = X \oplus Y = X \cdot Y' + X' \cdot Y$$

$$CO = X \cdot Y$$
- To add operands with more than one bit, carries between bit positions must be provided.


6. Combinational Practices

- Adders, Subtractors and ALUs (3) -

- The building block for this operation is called a full adder.
- Besides the addend-bit inputs X and Y, a full adder has a carry-bit input, CIN.
- The sum of the 3 bits can range from 0 to 3, which can still be expressed with just two output bits, S and COUT.
- The following equations can be written:

$$S = X \oplus Y \oplus CIN$$

 
$$COUT = X \cdot Y + X \cdot CIN + Y \cdot CIN$$



 6. Combinational Practices

- Adders, Subtractors and ALUs (4) -

- Two binary words, each with n bits, can be added using a ripple adder.
- A ripple adder is a cascade of n full-adders stages, each of which handles one bit.
- The carry input to the least significant bit (c_0) is usually set to 0.
- The carry output of each full adder is connected to the carry input of the next most significant full adder.



6. Combinational Practices


- Adders, Subtractors and ALUs (5) -

- The binary subtraction operation is analogous to binary addition.
- A full subtractor has inputs X (minuend), Y (subtrahend) and BIN (borrow in) and outputs D (difference) and BOUT (borrow out).
- The following equations can be written:
 - $D = X \oplus Y \oplus \text{BIN}$
 - $\text{BOUT} = X' \cdot Y + X' \cdot \text{BIN} + Y \cdot \text{BIN}$
- These equations are similar to the equations for a full adder.
 - $D = X \oplus Y \oplus \text{BIN}'$
 - $\text{BOUT} = X \cdot Y' + X \cdot \text{BIN}' + Y' \cdot \text{BIN}'$
- A full subtractor can be built from a full adder: $X - Y = X + Y' + 1$

 6. Combinational Practices

- Adders, Subtractors and ALUs (7) -

- An ALU is a combinational circuit that can perform several arithmetic and logical operations on a pair of-bit operands.
- The operation to be performed is specified by a set of function-select inputs.
- Typical MSI ALUs have 4-bit operands and three to five function-select inputs, allowing up to 32 different functions to be performed.
- A 74x181 IC has one 4-bit ALU.
- The operation performed by the 74x181 is selected by the M and S3-S0 inputs.



6. Combinational Practices

- Adders, Subtractors and ALUs (9) -


```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity vadder is
    port (
        A, B, C, D: in signed (7 downto 0);
        SEL: in std_logic;
        S: out signed (7 downto 0)
    );
end vadder;

architecture vadder_arch of vadder is
begin
    S <= A + B when SEL = '1' else C + D;
end vadder_arch;
```

6. Combinational Practices

- Adders, Subtractors and ALUs (6) -

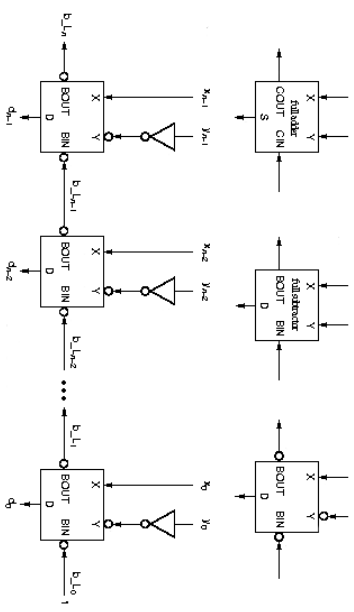

6. Combinational Practices


- Adders, Subtractors and ALUs (8) -

Inputs				Functions			
S3	S2	S1	S0	M=0 (arithmetic)	M=1 (logic)		
0	0	0	0	F = A minus 1 plus CIN	F = A'		
0	0	0	1	F = A · B minus 1 plus CIN	F = A' + B'		
0	0	1	0	F = A · B' minus 1 plus CIN	F = A' + B		
0	0	1	1	F = 1111 plus CIN	F = 1111		
0	1	0	0	F = A plus (A + B)' plus CIN	F = A' · B'		
0	1	0	1	F = A · B plus (A + B)' plus CIN	F = B'		
0	1	1	0	F = A minus (A + B)' plus CIN	F = A ⊕ B'		
0	1	1	1	F = A minus B minus 1 plus CIN	F = A ⊕ B		
1	0	0	0	F = A plus (A + B)' plus CIN	F = A' · B		
1	0	0	1	F = A · B plus (A + B)' plus CIN	F = B		
1	0	1	0	F = A + B plus CIN	F = A + B		
1	0	1	1	F = A plus A plus CIN	F = 0000		
1	1	0	1	F = A · B plus A plus CIN	F = A' · B'		
1	1	1	1	F = A plus A plus CIN	F = A · B		

 6. Combinational Practices


- Multipliers (1) -

- The traditional algorithm to multiply binary numbers uses shifts and adds to obtain the result.
- However, it is not the only solution to implement a multiplier.
- Given 2 n-bit inputs (X, Y), we can write a truth table that expresses the 2n-bit product P=X·Y as a combinational function of X and Y.
- Most approaches to combinational multipliers are based on the traditional shift-and-add algorithm.



6. Combinational Practices

- Multipliers (2) -

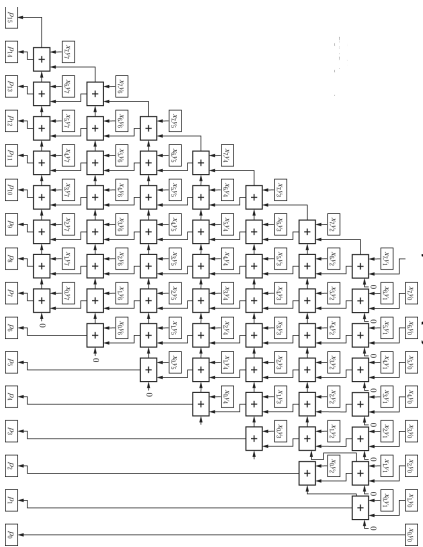

6. Combinational Practices

- Multipliers (3) -

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity vmul18x81 is
    port (
        X: in UNSIGNED (7 downto 0);
        Y: in UNSIGNED (7 downto 0);
        P: out UNSIGNED (15 downto 0)
    );
end vmul18x81;

architecture vmul18x81_arch of vmul18x81 is
begin
    P <= X * Y;
end vmul18x81_arch;
```