

# Módulo 4

## Introdução ao VHDL

## Modelação, Simulação e Síntese de Sistemas Digitais

*entity* – declara o interface de um componente;


*architecture* – descreve a realização de um componente;

- ❑ fluxo de dados
- ❑ estrutural
- ❑ comportamental

Uma entidade pode ter várias arquitecturas.
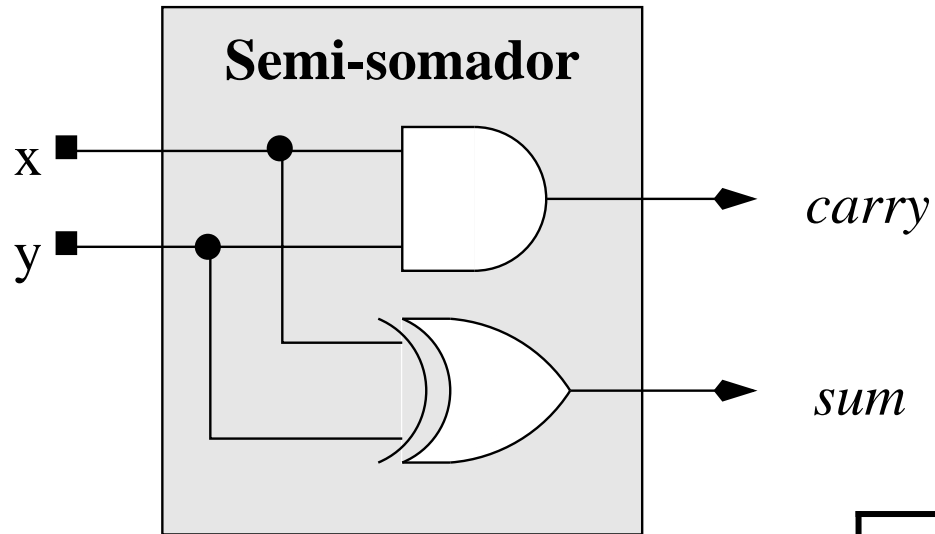
# Semi-Somador

- ❑ descrever em VHDL um semi-somador de 1 bit



x	y	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Semi-Somador

```
entity semi_somador is
  port (
    x, y : in bit;
    sum, carry : out bit );
end entity semi_somador;
```

nome  
modo  
tipo

nome da descrição

entidade descrita

```
architecture dflow of semi_somador is
  begin
    sum <= (x xor y) after 2 ns;
    carry <= (x and y) after 2 ns;
  end architecture dflow;
```

event triggered

atribuições concorrentes aos sinais com atraso de 2ns

# Semi-Somador

- ❑ substituir o tipo **bit** por **std\_logic**, definido no *package* **std\_logic\_1164** da biblioteca **IEEE**:


```
library IEEE;  
use      IEEE.std_logic_1164.all;
```

```
entity semi_somador is  
  port (  
    x,    y      : in  std_logic;  
    sum, carry : out std_logic );  
end entity semi_somador;
```

```
architecture dflow of semi_somador is  
  begin  
    sum    <= (x xor y) after 2 ns;  
    carry <= (x and y) after 2 ns;  
  end architecture dflow;
```

 
# Semi-Somador

- ilustração do funcionamento do semi-somador


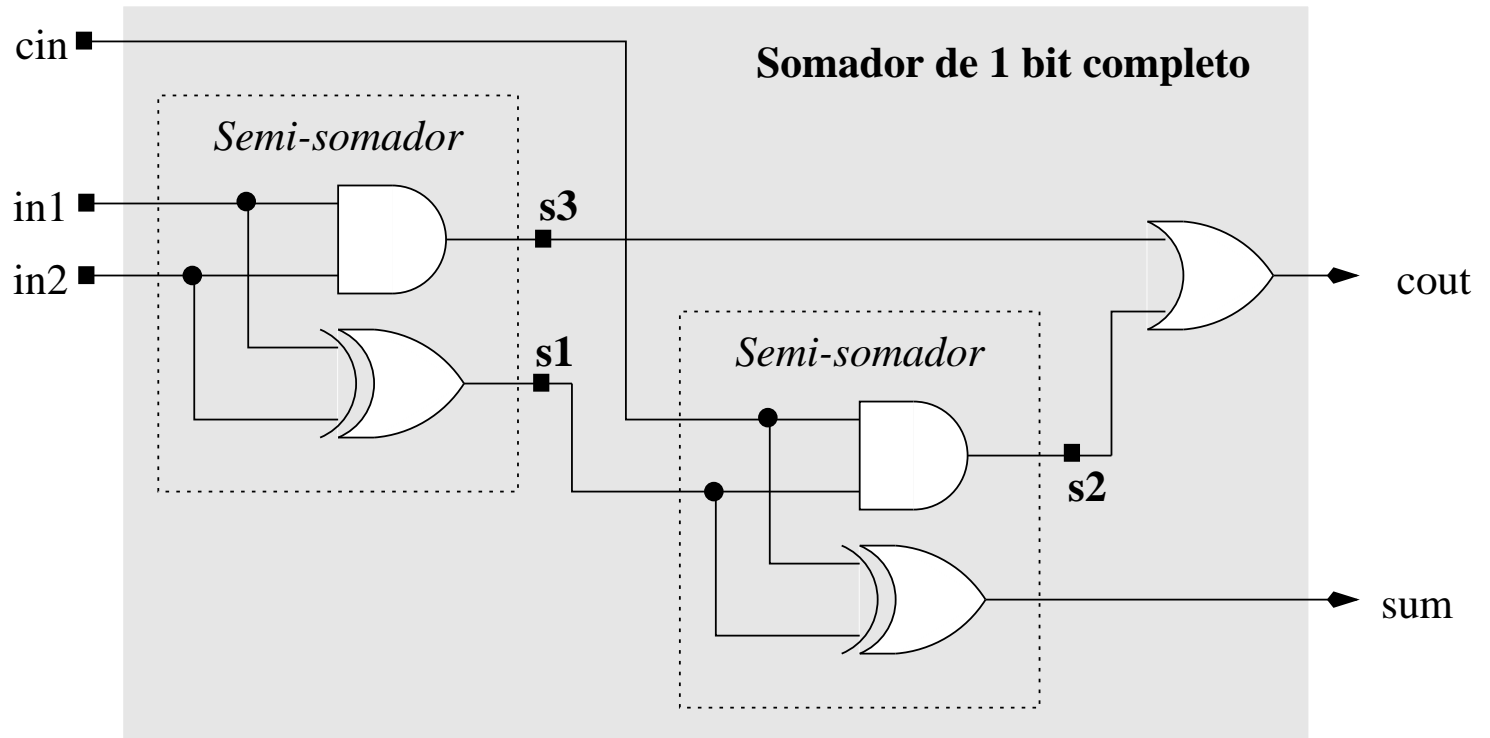
# Somador Completo

- ❑ descrever em VHDL um somador de 1 bit



# Somador Completo

```
library IEEE;  
use      IEEE.std_logic_1164.all;  
  
entity somador is  
  port (  
    in1, in2, cin : in  std_logic;  
    sum, cout      : out std_logic );  
end entity somador;
```



# Somador Completo

```

library IEEE;
use      IEEE.std_logic_1164.all;

entity somador is
  port (
    in1, in2, cin  : in  std_logic;
    sum, cout      : out std_logic );
end entity somador;

architecture estrutural of somador is

  component semi_somador is
    port (
      x, y      : in  std_logic;
      sum, carry : out std_logic );
  end component semi_somador;

```

```

signal s1, s2, s3 : std_logic;
constant atraso   : time := 2 ns;

begin

  SUM1: semi_somador
    port map (
      x => in1  ,
      y => in2  ,
      sum => s1  ,
      carry => s3 );

  SUM2: semi_somador
    port map (
      x => cin   ,
      y => s1    ,
      sum => sum ,
      carry => s2 );

  FIN: cout <= s3 or s2 after atraso;

end architecture estrutural ;

```

# Somador Completo : alternativa *data flow*

```
architecture dflow of somador is
```

```
    signal s1, s2, s3 : std_logic;
```

```
    constant atraso    : time := 2 ns;
```

```
begin
```

```
    X1: s1    <= (in1 xor in2) after atraso;
```

```
    A1: s2    <= (cin and  s1) after atraso;
```

```
    A2: s3    <= (in1 and in2) after atraso;
```

```
    X2: sum   <= (s1 xor cin) after atraso;
```

```
    O1: cout  <= (s2 or   s3) after atraso;
```

```
end architecture dflow ;
```

# Descrição comportamental

Descrição comportamental  $\Leftrightarrow$  algorítmica

A sequência de instruções aparece dentro de um *process*

Um processo tem uma lista de sensibilidade, indicando quais os sinais que activam o processo quando se registar um evento

Um processo pode ter variáveis.

```
process (A,B)
  variable T1, T2: BIT;
begin
  .....      -- sequência de instruções
end
```

# Somador Completo : descrição comportamental

```
architecture processos of somador is
    signal s1, s2, s3 : std_logic;
    constant atraso    : time := 2 ns;
begin

    SS1: process (in1,in2) is
        begin
            s1  <= (in1 xor in2) after atraso;
            s3  <= (in1 and in2) after atraso;
        end process SS1;


    SS2: process (s1, cin) is
        begin
            s2  <= (cin and s1) after atraso;
            sum <= (s1 xor cin) after atraso;
        end process SS2;

    O1: cout <= (s2 or s3) after atraso;

end architecture processos ;
```
 
# Multiplexador 4:1

- ❑ descrever em VHDL um **multiplexador 4:1**



# Multiplexador 4:1

```
library IEEE;
use      IEEE.std_logic_1164.all;

entity mux4to1 is
  port (
    in0, in1, in2, in3 : in  std_logic;
    s : in std_logic_vector (1 downto 0);
    z      : out std_logic );
end entity mux4to1 ;
```

# Multiplexador 4:1 - descrição *data flow*

**architecture dflow of mux4to1 is**

```
constant atraso : time := 2 ns;
```

```
begin
```

```
z <= in0 after atraso when s="00" else  
    in1 after atraso when s="01" else  
    in2 after atraso when s="10" else  
    in3 after atraso when s="11" else  
    '0' after atraso ;
```

```
end architecture dflow;
```

# Multiplexador 4:1 - descrição comportamental [1]

```
architecture comportamental of mux4to1 is
    constant atraso : time := 2 ns;
begin
    process (s, in3, in2, in1, in0) is
    begin
        if s="00" then
            z <= in0 after atraso ;
        elsif s="01" then
            z <= in1 after atraso ;
        elsif s="10" then
            z <= in2 after atraso ;
        elsif s="11" then
            z <= in3 after atraso ;
        else
            z <= '0' after atraso ;
        end if;
    end process;
end architecture comportamental ;
```



# Multiplexador 4:1 - descrição comportamental [2]

```
architecture comportamental2 of mux4to1 is
    constant atraso : time := 2 ns;
begin
    process (s, in3, in2, in1, in0)
    begin
        case s is -- diferente s(0 to 1)
            when "00" =>
                z <= in0 after atraso ;
            when "01" =>
                z <= in1 after atraso ;
            when "10" =>
                z <= in2 after atraso ;
            when "11" =>
                z <= in3 after atraso ;
            when others =>
                z <= '0' after atraso ;
        end case;
    end process;
end architecture comportamental2 ;
```

# Multiplexador 4:1 - descrição comportamental [3]

```
architecture comportamental3 of mux4to1 is
    constant atraso : time := 2 ns;
begin
    process(s,in0,in1,in2,in3)
        variable value : integer := 0;
        begin
            if s(0)='1' then value := value + 1; end if;
            if s(1)='1' then value := value + 2; end if;
            case value is
                when 0 => z <= in0 after atraso;
                when 1 => z <= in1 after atraso;
                when 2 => z <= in2 after atraso;
                when 3 => z <= in3 after atraso;
                when others => z <= '0';
            end case;
        end process;
end architecture comportamental3 ;
```

# Exercício

Pretende-se modelar um componente que indique a paridade de 3 bits, isto é, coloque a sua saída a 1 se o número de 1's nas 3 entradas for par.

1. Faça a tabela de verdade do circuito e obtenha a expressão booleana simplificada.
2. Faça a modelação *data flow* em VHDL
3. Faça a modelação comportamental
4. Descreva estruturalmente um circuito que detecte a paridade de 6 bits usando o componente desenvolvido nas alíneas anteriores.
5. Simule o detector de paridade 3 para ambas as arquitecturas.

## Exercício: alínea 2

```
library IEEE;
use      IEEE.std_logic_1164.all;

entity par3 is
  port (
    e0, e1, e2 : in std_logic;
    z : out std_logic );
end entity par3 ;
```

## Exercício: alínea 2

```
architecture dflow of par3 is
```

```
signal s1, s2, s3, s4 : std_logic;
```

```
signal ne0, ne1, ne2: std_logic;
```

```
constant atraso    : time := 2 ns;
```

```
begin
```

```
    n1: ne0 <= not e0 after atraso;
```

```
    n2: ne1 <= not e1 after atraso;
```

```
    n3: ne2 <= not e2 after atraso;
```

```
    m1: s1 <= (ne0 and ne1 and ne2) after atraso;
```

```
    m2: s2 <= (ne0 and e1 and e2) after atraso;
```

```
    m3: s3 <= (e0 and ne1 and e2) after atraso;
```

```
    m4: s4 <= (e0 and e1 and ne2) after atraso;
```

```
    final: z <= (s1 or s2 or s3 or s4) after atraso;
```

```
end architecture dflow ;
```

## Exercício: alínea 3

```
architecture beha of par3 is
begin
process (e0,e1,e2)
variable contador,resto:integer;
begin
    contador := 0;
    if e0 = '1' then contador := contador+1;
    end if;
    if e1 = '1' then contador := contador+1;
    end if;
    if e2 = '1' then contador := contador+1;
    end if;
    resto := contador rem 2;
    if resto=1 then z <= '0';
    else z <= '1';
    end if;
    end process;
end architecture beha ;
```

# Exercício: alínea 4

```
library IEEE;
use      IEEE.std_logic_1164.all;

entity par6 is
  port (
    e : in  std_logic_vector(0 to 5);
    par : out std_logic );
end entity par6;

architecture estrutural of par6 is

  component par3 is
  port (
    e0, e1, e2 : in std_logic;
    z : out std_logic );
  end component par3 ;

  signal s1, s2, s3 : std_logic;
  constant atraso : time := 2 ns;
```

```
begin
  PAR3_1: par3
  port map (
    e0 => e(0),
    e1 => e(1),
    e2 => e(2),
    z => s1);

  PAR3_2: par3
  port map (
    e0 => e(3),
    e1 => e(4),
    e2 => e(5),
    z => s2);


  s3 <= (s1 xor s2) after atraso;
  par <= not s3 after atraso;

end architecture estrutural;
```
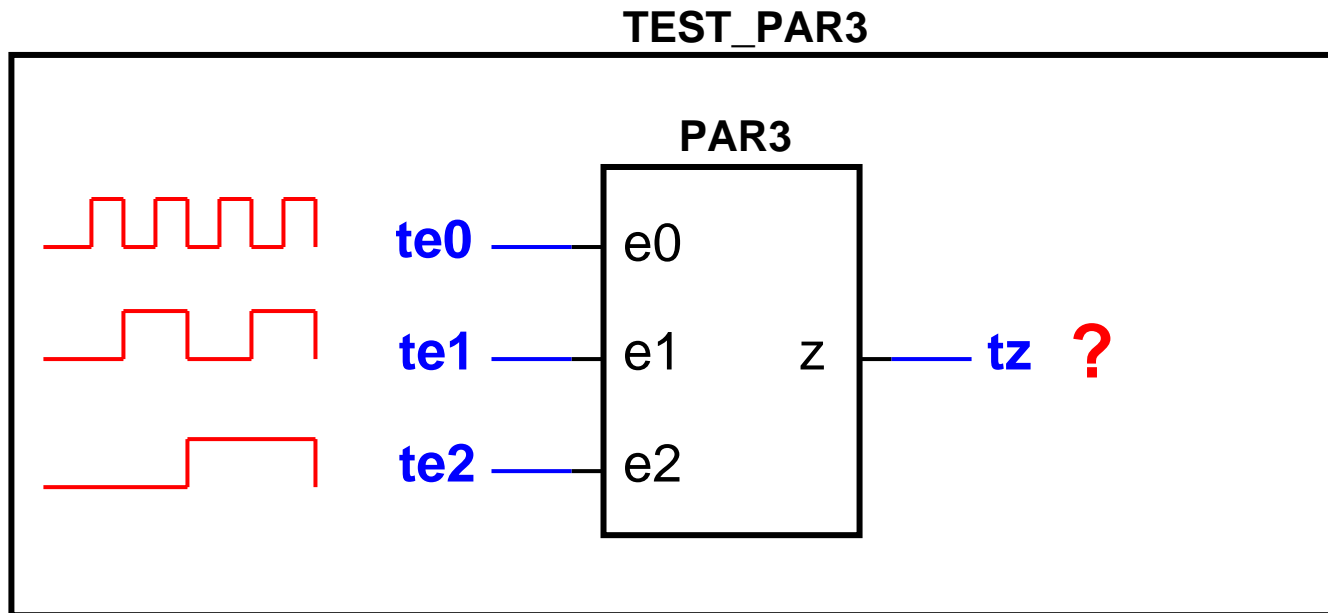
## Exercício: alínea 5

Para fazer uma simulação é necessário desenvolver uma bancada de teste (*test bench*).

Este componente não tem entradas nem saídas, mas os seus sinais internos correspondem aos sinais de entrada/saída do componente a testar. São estes sinais que podemos modificar e observar.





# Exercício: alínea 5

```

library IEEE;
use      IEEE.std_logic_1164.all;

entity test_par3 is
end entity test_par3;

architecture tstbench of test_par3 is

component par3 is
  port (
    e0, e1, e2  : in std_logic;
    z          : out std_logic );
end component par3;

  signal te0   : std_logic := '0';
  signal te1   : std_logic := '0';
  signal te2   : std_logic := '0';
  signal tz    : std_logic ;

begin
  -- comportamento dos sinais de entrada

```

```

process (te0) is          -- te0
begin
  if te0='1' then
    te0 <= '0' after 10ns;
  elsif te0='0' then
    te0 <= '1' after 10ns;
  end if;
end process;

process (tel) is         -- tel
begin
  if tel='1' then
    tel <= '0' after 20ns;
  elsif tel='0' then
    tel <= '1' after 20ns;
  end if;
end process;

process (te2) is        -- cin
begin
  if te2='1' then
    te2 <= '0' after 40ns;
  elsif te2='0' then
    te2 <= '1' after 40ns;
  end if;
end process;

```


## Exercício 4 : *testbench*

```
-- instanciar o sistema a testar
PROC_PAR3: entity par3(dflow)
  port map (
    e0    => te0  ,
    e1    => te1  ,
    e2    => te2  ,
    z     => tz   );

end architecture tstbench ;
```
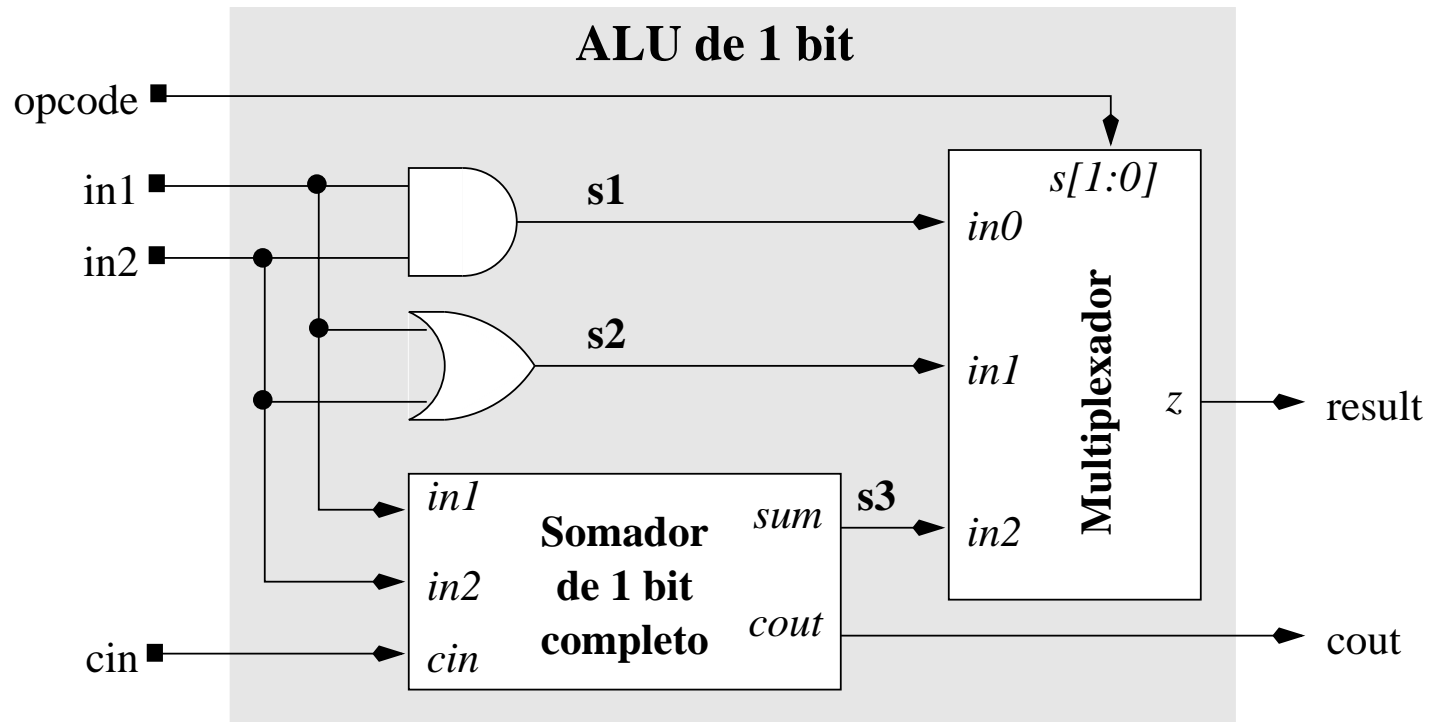
## Exercício 4 alínea 6

- descrever e simular em VHDL uma ALU de 1 bit



## Exercício 4 alínea 6 : somador de 1 bit

```
library IEEE;
use      IEEE.std_logic_1164.all;

entity somador is
  port (
    in1, in2, cin : in  std_logic;
    sum, cout      : out std_logic );
end entity somador;

architecture dflow of somador is

  signal s1, s2, s3 : std_logic;
  constant atraso   : time := 2 ns;

begin

  X1: s1  <= (in1 xor in2) after atraso;
  A1: s2  <= (cin and  s1) after atraso;
  A2: s3  <= (in1 and in2) after atraso;
  X2: sum <= (s1  xor cin) after atraso;
  O1: cout <= (s2  or   s3) after atraso;

end architecture dflow ;
```

## Exercício 4 alínea 6: multiplexador

```
library IEEE;
use      IEEE.std_logic_1164.all;

entity mux3to1 is
  port (
    in0, in1, in2 : in std_logic;
    s : in std_logic_vector (1 downto 0);
    z : out std_logic );
end entity mux3to1 ;
```

```
architecture funcional_case of mux3to1 is
  constant atraso : time := 2 ns;
begin
  process (s, in2, in1, in0)
  begin
    case s(1 downto 0) is
      when "00" =>
        z <= in0 after atraso ;
      when "01" =>
        z <= in1 after atraso ;
      when "10" =>
        z <= in2 after atraso ;
      when others =>
        z <= '0' after atraso ;
    end case;
  end process;
end architecture funcional_case;
```