OF = overflow bit
SW = Switch (select addition or subtraction)

Figure 8.6 Block Diagram of Hardware for Addition and Subtraction